



Name: Yaseen Reyad Hassan

ID : 1320221531

Course: Advanced Electrical and Electronic Circuits

Instructor: Dr. Mohamed Kamal Naeem

Real-World Design and Analysis of an AC Filter Circuit

1. Theoretical Background

Sinusoidal Steady-State

Sinusoidal steady-state analysis is a powerful method for analyzing linear electric circuits driven by sinusoidal sources (e.g., sine waves) after all transient effects have died out. In this state, all voltages and currents in the circuit are also sinusoidal with the same frequency as the source, but with different amplitudes and phase angles. This technique simplifies the analysis of time-varying AC circuits by transforming the problem from a differential equation in the time domain to an algebraic equation in the frequency domain.

Phasor Concept and Importance

A **phasor** is a complex number that represents a sinusoidal voltage or current. It captures both the **amplitude** and **phase angle** of the sinusoid, but not its frequency. The magnitude of the phasor corresponds to the amplitude of the signal, and its angle corresponds to the phase shift relative to a reference.

For example, a voltage $v(t) = V_m \cos(\omega t + \phi)$ is represented in phasor form as $V = V_m \angle \phi$.

The importance of phasors lies in their ability to transform the complex calculus involved in AC analysis into simple algebra. Operations like differentiation and integration become multiplication and division by $j\omega$, making circuit analysis significantly easier.

Impedance in the Phasor Domain

Impedance (Z) is the total opposition a circuit element presents to alternating current. It's a complex number that generalizes the concept of resistance to AC circuits.

- **Resistor (R):** The impedance of a resistor is simply its resistance, which is a real number and doesn't change with frequency.

$$Z_R = R$$

- **Inductor (L):** An inductor's impedance is purely imaginary and increases with frequency.

$$Z_L = j\omega L$$

- **Capacitor (C):** A capacitor's impedance is also purely imaginary but decreases with frequency.

$$Z_C = \frac{1}{j\omega C}$$

AC Filters and Their Types

An **AC filter** is an electronic circuit designed to pass specific frequencies while blocking or attenuating others. They are essential for signal processing, noise reduction, and many other applications. The main types of filters are:

- **Low-Pass Filter (LPF):** Passes frequencies below a certain **cutoff frequency** (f_c) and blocks those above it.
- **High-Pass Filter (HPF):** Passes frequencies above the cutoff frequency and blocks those below it.
- **Band-Pass Filter (BPF):** Passes a specific band of frequencies and blocks all others.
- **Band-Stop Filter (BSF) or Notch Filter:** Blocks a specific band of frequencies and passes all others.

Frequency Response and Bode Plot

The **frequency response** of a circuit describes how the circuit's output behaves as a function of the input signal's frequency. It's a crucial tool for analyzing AC circuits, especially filters. It's typically represented by two plots: a **magnitude plot** (or gain) and a **phase plot**.

A **Bode plot** is a specific way of graphing the frequency response. It consists of these two plots:

1. **Magnitude Plot:** Plots the logarithm of the gain (in decibels, dB) versus the logarithm of the frequency. This allows a wide range of frequencies to be shown on a single graph.
2. **Phase Plot:** Plots the phase angle (in degrees) versus the logarithm of the frequency.

Bode plots are particularly useful for filter design and analysis because they provide a clear visual representation of the filter's behavior. They show the filter's **passband** (where the gain is flat), **stopband** (where the gain decreases), and the **roll-off** rate, which is the slope of the magnitude plot in the stopband.


2. Real Filter Circuit Analysis

Audio Crossover Low-Pass Filter (LC Filter):

A common low-pass filter used in a passive audio crossover network for a speaker system is an **LC filter**. This specific example uses an inductor and a capacitor to create a second-order filter.

Circuit Description and Diagram

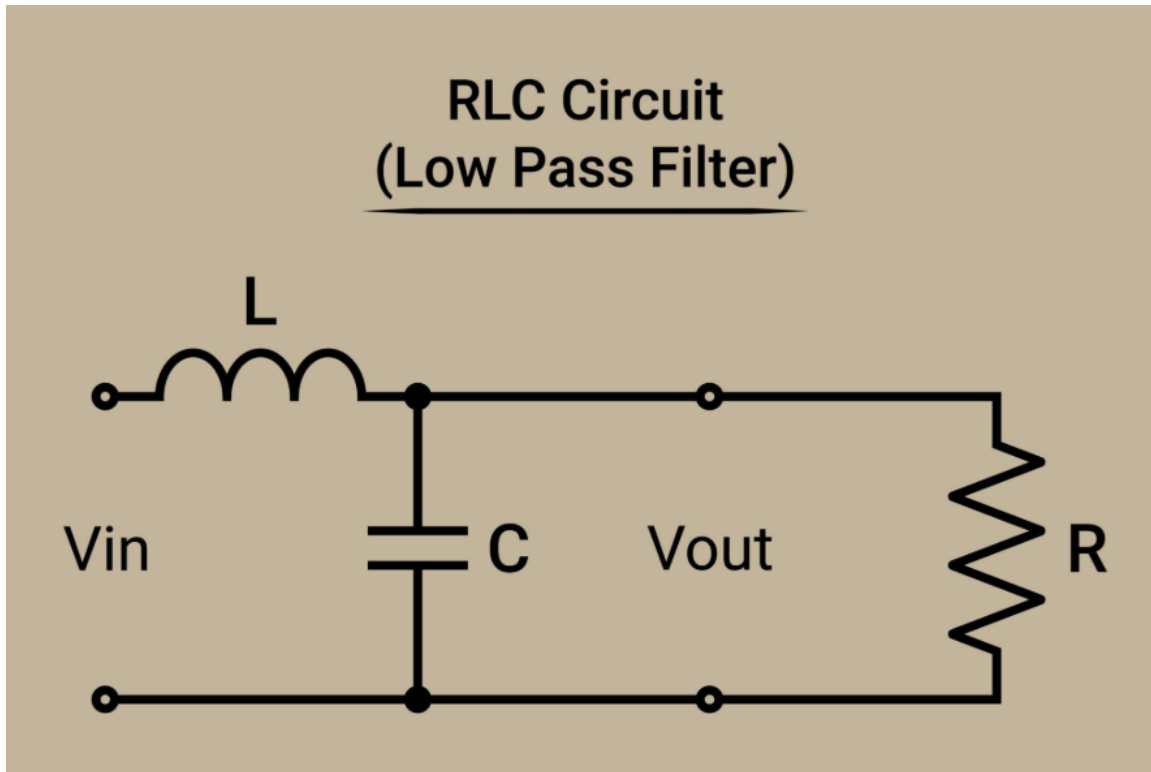The filter is a second-order **LC filter**. It uses a single inductor (L) and a single capacitor (C) to achieve a sharper cutoff than a simple RC filter. The input signal comes from an audio amplifier, and the output is connected to a woofer (a low-frequency speaker), which we will model as a resistor (R_L).



Component Values

- **Type of Filter:** Second-order passive **Low-Pass Filter (LPF)**.
- **Components:**
 - **Inductor (L):** $L=1.0 \text{ mH}$
 - **Capacitor (C):** $C=100 \text{ }\mu\text{F}$
 - **Speaker (Load):** The speaker's impedance can be modeled as a resistor (R) for this analysis. Let's assume a typical speaker impedance of $R=8 \text{ }\Omega$.

Transfer Function Derivation

The transfer function, $H(j\omega)$, is the ratio of the output voltage phasor, V_{out} , to the input voltage phasor, V_{in} .

Using the voltage divider rule in the phasor domain:

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_C \parallel Z_R}{Z_L + (Z_C \parallel Z_R)}$$

First, find the parallel impedance of the capacitor and speaker:

$$Z_{out} = Z_C \parallel Z_R = \frac{Z_C Z_R}{Z_C + Z_R} = \frac{(-\frac{j}{\omega C})R}{-\frac{j}{\omega C} + R} = \frac{-jR}{1 + j\omega CR}$$

Now, substitute this into the voltage divider formula:

$$H(j\omega) = \frac{\frac{-jR}{1 + j\omega CR}}{j\omega L + \frac{-jR}{1 + j\omega CR}} = \frac{-jR}{j\omega L(1 + j\omega CR) - jR} = \frac{-jR}{j\omega L - \omega^2 LCR - jR}$$

To simplify, let's divide the numerator and denominator by jR :

$$H(j\omega) = \frac{-1}{\frac{\omega L}{R} - j\omega^2 LC - 1}$$

This is the transfer function for the circuit.

Cutoff Frequency (f_c)

The cutoff frequency (f_c) for a second-order filter is where the gain drops to $1/\sqrt{2}$ (or approximately -3 dB) of its maximum value. For a second-order LC filter, the natural resonance frequency, f_0 , often approximates the cutoff frequency, especially when damping is low.

The resonant frequency is given by: $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Using the given values:

$$f_0 = \frac{1}{2\pi\sqrt{(1.0 \times 10^{-3} \text{ H}) \times (100 \times 10^{-6} \text{ F})}} = 503.29 \text{ Hz}$$

This frequency is approximately the cutoff frequency for this filter.

MATLAB code for Cutoff Frequency Calculation:

```
% Define component values
L = 1.0e-3; % Inductance in Henries
C = 100e-6; % Capacitance in Farads
% Calculate the cutoff frequency (resonant frequency)
f_cutoff = 1 / (2 * pi * sqrt(L * C));
% Display the result
fprintf('The cutoff frequency is approximately %.2f Hz\n', f_cutoff);
```

Result: The cutoff frequency is approximately **503.29 Hz**.


Bode Plot

The Bode plot consists of two graphs: one for the magnitude (gain) and one for the phase angle of the transfer function, both plotted against frequency on a logarithmic scale.

MATLAB code for Bode Plot Generation:

```
% Define component values
L = 1.0e-3; % Henries
C = 100e-6; % Farads
RL = 8; % Ohms
% Define the transfer function H(s)
s = tf('s');
H_s = RL / ((L*RL*C)*s^2 + (L)*s + RL);
% Generate the Bode plot
figure;
bode(H_s);
grid on;
title('Bode Plot of a Low-Pass Filter');
```

Result:

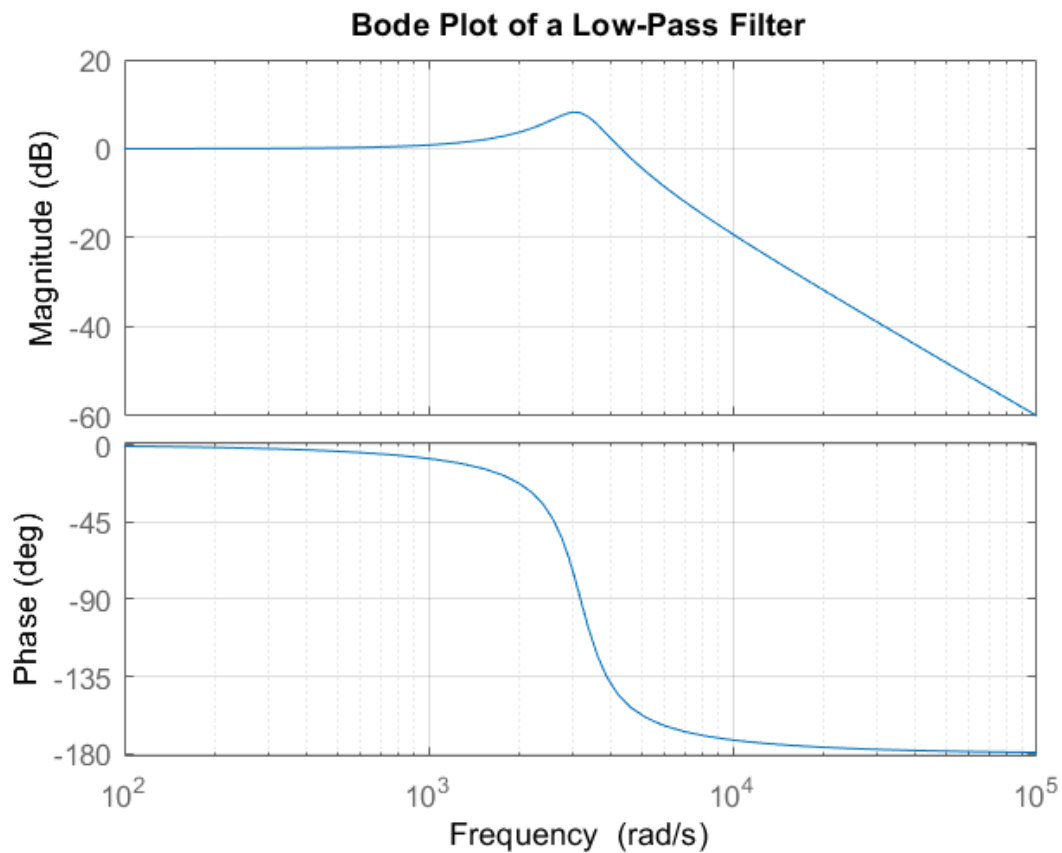

- **Magnitude Plot (Gain):**

At very low frequencies ($\omega \ll \omega_0$), the inductor's impedance is negligible ($Z_L \rightarrow 0$) and the capacitor's impedance is very high ($Z_C \rightarrow \infty$). The circuit acts like a simple wire, so the output voltage equals the input voltage, resulting in a gain of 1 (0 dB). As the frequency increases, the inductor's impedance grows and the capacitor's impedance shrinks. At the cutoff frequency, the gain starts to drop. For a second-order filter, the gain rolls off at a rate of **-40 dB per decade** in the stopband.

- **Phase Plot:**

At low frequencies, the phase shift is close to 0° . At the cutoff frequency, the phase shift is -90° . At high frequencies, the phase shift approaches -180° . The phase change occurs gradually, but most of the change happens around the cutoff frequency.

Phasor Relationships

- **Low Frequencies ($\omega \ll f_c$):**

The capacitor's impedance is much larger than the resistor's, so it acts like an open circuit. The inductor's impedance is negligible, so it acts like a short circuit. The circuit is primarily resistive, and the current and voltage are mostly in phase.

- **High Frequencies ($\omega \gg f_c$):**

The capacitor's impedance is very small, so it acts like a short circuit, shunting the high-frequency current to ground. The inductor's impedance is very large, blocking the high-frequency current. The output voltage across the capacitor is very small. The voltage across the inductor leads the current through it by 90° , and the current through the capacitor leads the voltage across it by 90° .

3. Real-World Application

Application in an Audio Speaker Crossover Network

This LC low-pass filter is a crucial part of a **passive crossover network** inside a two-way speaker cabinet. A speaker crossover is a circuit that splits an incoming audio signal into multiple frequency bands and directs them to the appropriate speaker drivers. The **woofer**, a large speaker, is designed to reproduce low-frequency bass sounds, while the **tweeter**, a smaller speaker, handles high-frequency treble sounds.

The low-pass filter is placed in the signal path leading to the woofer. Its purpose is to filter out the high-frequency content of the audio signal before it reaches the woofer.

- **Passed Signal:** The filter allows low-frequency signals (below 500 Hz) to pass through to the woofer.
- **Blocked Signal:** It significantly attenuates or blocks high-frequency signals, preventing them from reaching the woofer.

This is important because woofers are physically large and heavy, making them inefficient at reproducing high-frequency vibrations. Trying to drive a woofer with high-frequency signals results in poor sound quality, distortion, and could even damage the speaker over time due to excessive and inefficient movement.

Technical Justification

The low-pass filter ensures that the woofer operates within its optimal frequency range. By filtering out high frequencies, the filter ensures the woofer cone moves more efficiently and accurately, producing clear, powerful bass without distortion. The filter's **cutoff frequency** is chosen to create a smooth transition between the woofer and the tweeter, which would have a corresponding high-pass filter. This creates a seamless, full-range sound experience.

What would happen without the filter?

Without a low-pass filter, the full-range audio signal would be sent to the woofer. The woofer would try to reproduce all frequencies, including the high ones. This would lead to several problems:

1. **Poor Sound Quality:** The woofer's inability to vibrate quickly enough to reproduce high frequencies would result in muddy, distorted, and unfocused sound.
2. **Damaged Speaker:** The woofer's voice coil would be forced to move rapidly and erratically, generating excessive heat and potentially leading to premature failure.
3. **Inefficient Power Usage:** Power would be wasted trying to drive the woofer with signals it can't reproduce effectively, reducing the overall efficiency of the speaker system.

4. Resonance Insight

Resonance in the LC Filter

Yes, a filter circuit containing both an inductor (L) and a capacitor (C) can exhibit **resonance**. Resonance occurs in an RLC circuit when the inductive reactance ($X_L = \omega L$) and capacitive reactance ($X_C = \frac{1}{\omega C}$) are equal in magnitude.

At the resonance frequency (f_0), the impedance of the inductor and capacitor cancel each other out, making the circuit appear purely resistive from the input terminals.

The resonance frequency is given by the formula: $f_0 = \frac{1}{2\pi\sqrt{LC}}$

This is the same frequency calculated earlier for the low-pass filter's cutoff. At this frequency, the voltage across the capacitor (the output voltage) can peak, particularly if the damping (resistance) is low.

Quality Factor (Q) and Selectivity

The **quality factor (Q)** is a dimensionless parameter that describes how underdamped a resonant circuit is. It quantifies the sharpness of the resonance peak. For our series RLC circuit, a higher Q factor means the resonance peak is taller and narrower.

For a series RLC circuit, the quality factor is given by:

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Using the values from the low-pass filter example:

$$Q = \frac{2\pi f_0 L}{R} = \frac{2\pi(503.29 \text{ Hz})(1.0 \times 10^{-3} \text{ H})}{8 \Omega} = 0.395$$

A low Q value (like this one) indicates a well-damped circuit, meaning the resonance peak is broad and not very pronounced.

Selectivity is the ability of a resonant circuit to distinguish between a desired frequency and other frequencies. It is directly related to the Q factor. A higher Q factor results in higher selectivity, as the filter will have a narrower bandwidth and be more selective in which frequencies it passes. In this low-pass filter application, we're not using the resonance to select a specific frequency band, so selectivity is not a primary design concern, but the Q factor still helps us understand the shape of the filter's frequency response curve. A low Q leads to a more gradual roll-off, which can be desirable for a smooth crossover.